

# Network Analysis and Synthesis

Tutorial

ECL 1022


# Network Theorems

(as explained in the class)



read it to revise it for clearing any doubts  
Any doubts will be cleared in the next class

# Networks to illustrate Thevenin theorem


Original (Given) Circuit

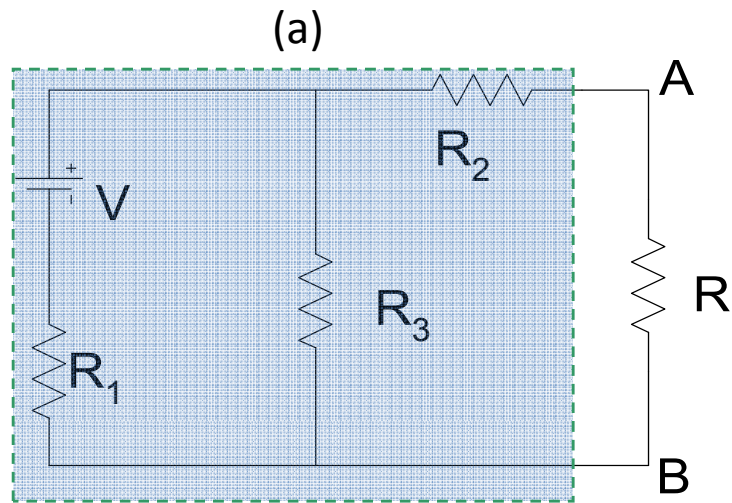

Step I and Step II

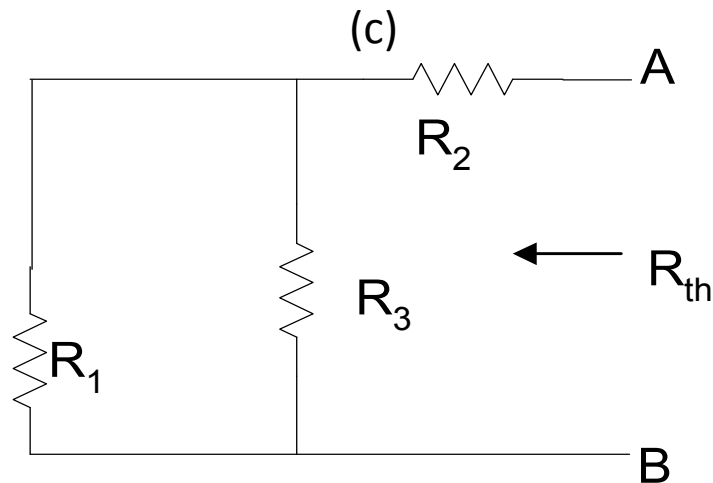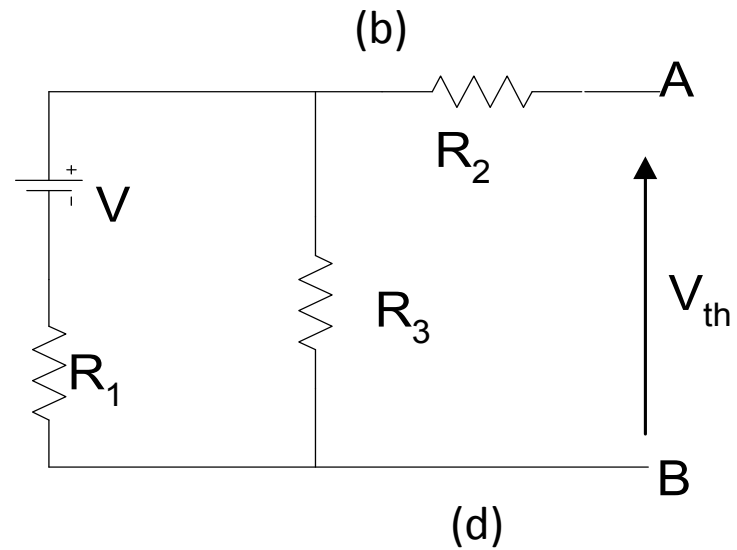


Step III

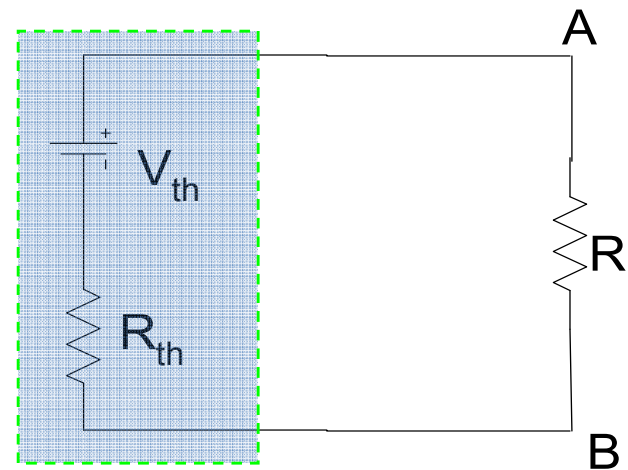

Thevenin's Equivalent Circuit

# Norton's Theorem

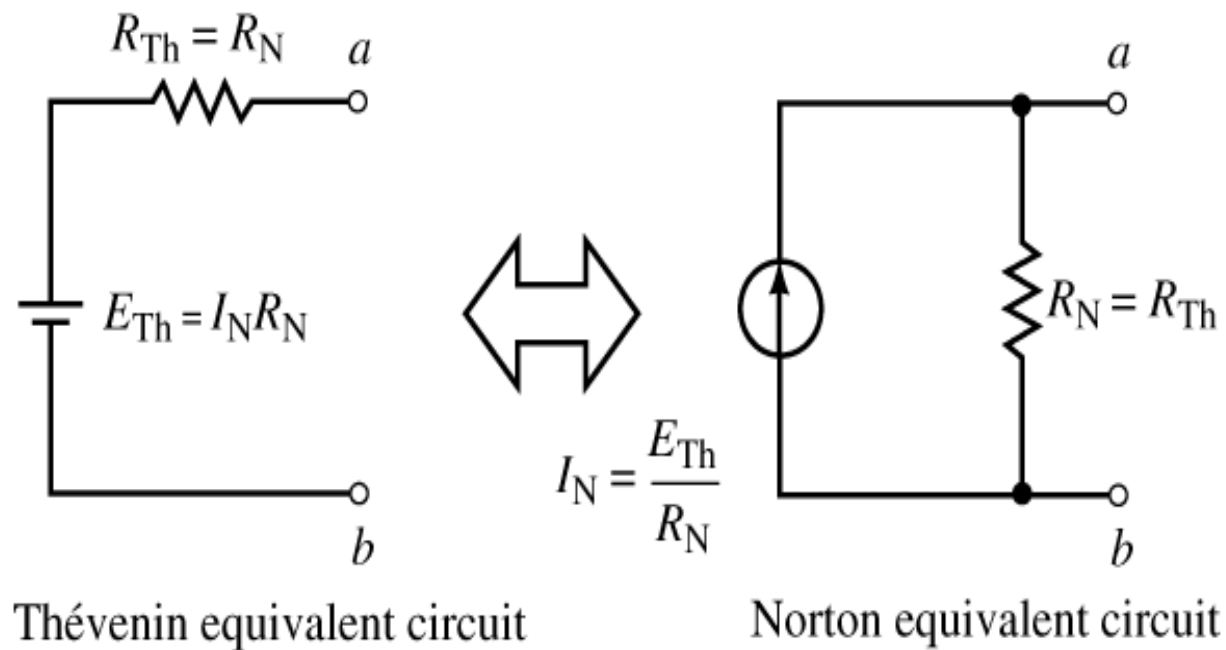

***$E_{th}$  and  $V_{th}$  are used interchangeably***

Q. Calculate the current through  $8\Omega$  for the network shown in figure (a) (**THEVENIN THEOREM**)

## Solution

**Step I:** Remove  $8\Omega$  and replace it with open-circuit (oc) as shown in figure (b)

**Step II:** With  $8\Omega$  disconnected as in figure (b), find  $V_{oc}$  using superposition theorem as in figure (c)

Contribution due to  $E_1$  (i.e.  $E_{th}=V_{th}=V_{oc}$ )

$$\Rightarrow V_{th1} = \frac{12\Omega(18V)}{6\Omega + 12\Omega + 4\Omega} = \frac{216}{22} = 9.82V$$


Now contribution due to current source as in figure (d);

Applying current divider rule:


$$I' = \frac{4\Omega(2A)}{4\Omega + 18\Omega} = 0.364A$$

$$\Rightarrow V_{th2} = -I'(12\Omega) = -4.37V$$
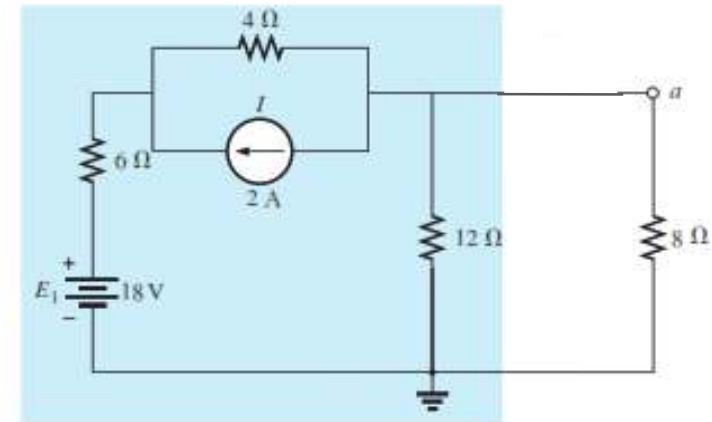
$$\Rightarrow V_{th} = V_{th1} + V_{th2} = 9.82V - 4.37V = 5.45V$$



(a)

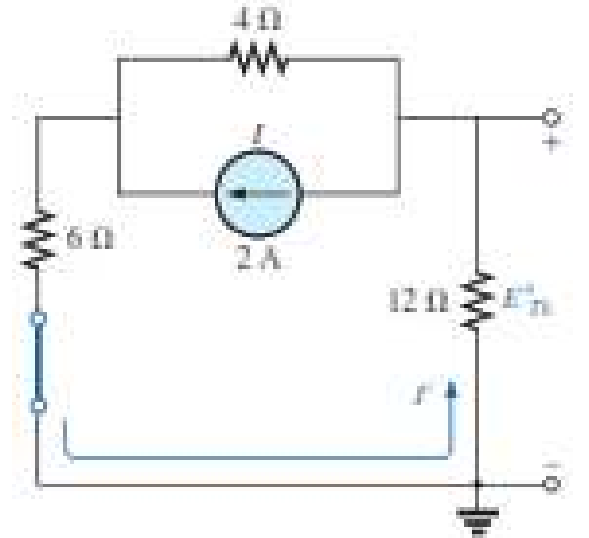

(b)

continue


**Step III:** Remove the source and replace it with short circuit, and open circuit respectively, and determine the internal resistance ( $R_{th}$ ) as in figure (e)

$$R_{th} = 12\Omega \parallel (4\Omega + 6\Omega) = 12\Omega \parallel 10\Omega = 5.45\Omega$$


**Step IV:** Replace the network with  $V=5.2V$  and  $R_{th}=1.2$ , then the at terminal CD,  $R_3$ , thus the current

$$I = \frac{5.45V}{5.45\Omega + 8\Omega} = 0.4A$$


$$V_l = 0.4A * 8\Omega = 3.2V$$

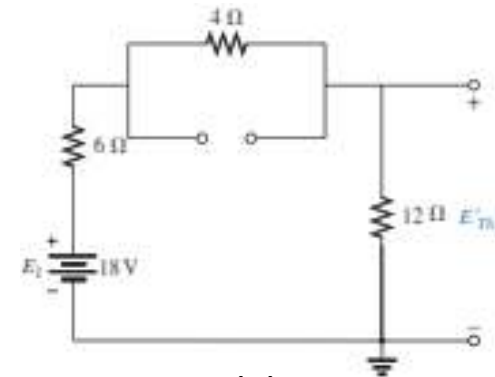

(c)

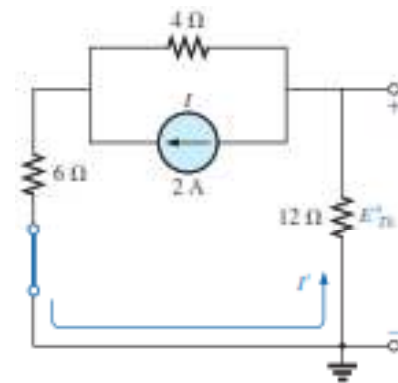

(d)

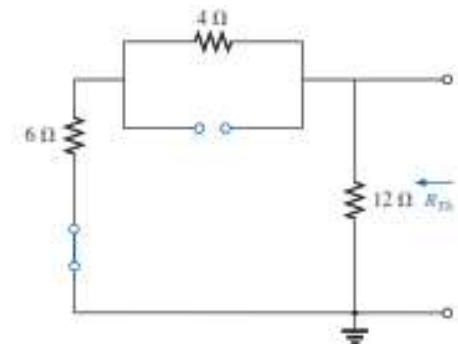


(e)

Q. Calculate the current through  $9\Omega$  for the network shown in figure (a) (**NORTON THEOREM**)
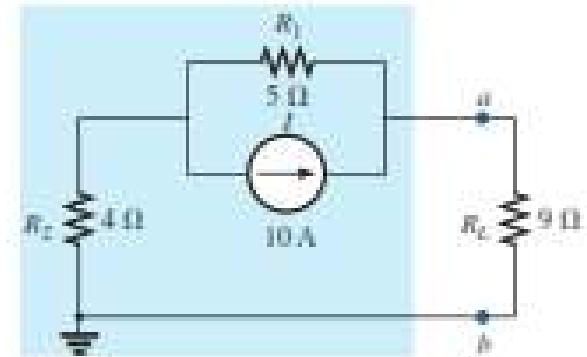
### **Solution**


**Step I:** Remove  $9\Omega$  and replace it with short-circuit (sc) as shown in figure (b)



(a)

**Step II:** With  $9\Omega$  disconnected (sc) as in figure (b), find  $I_N$  (norton's current) using current divider rule.
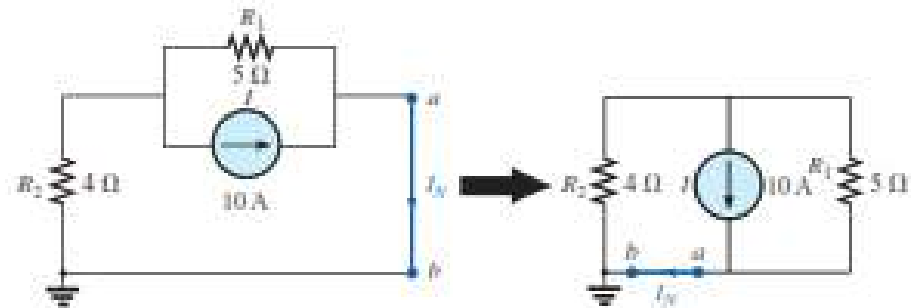
$$\Rightarrow I_N = \frac{5\Omega(10 A)}{5\Omega + 4\Omega} = \frac{50 A}{9} = 5.56 A$$



(b)


continue

**Step III:** Remove the source(s) and replace it with short circuit, and open circuit respectively, and determine the internal resistance ( $R_N$ ) same way as done for  $R_{th}$  as in figure (c)

$$R_N = 5\Omega + 4\Omega = 9\Omega$$

**Step IV:** Norton's Equivalent circuit in figure (d)

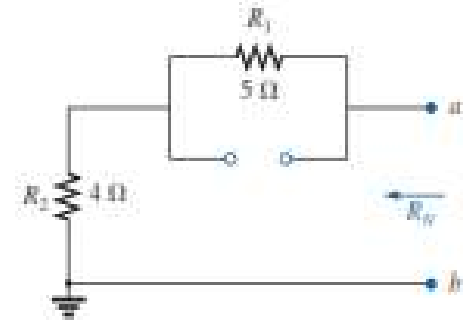Using current divider rule calculate the current in  $9\Omega$ .




(c)



(d)



# Current Divider Rule

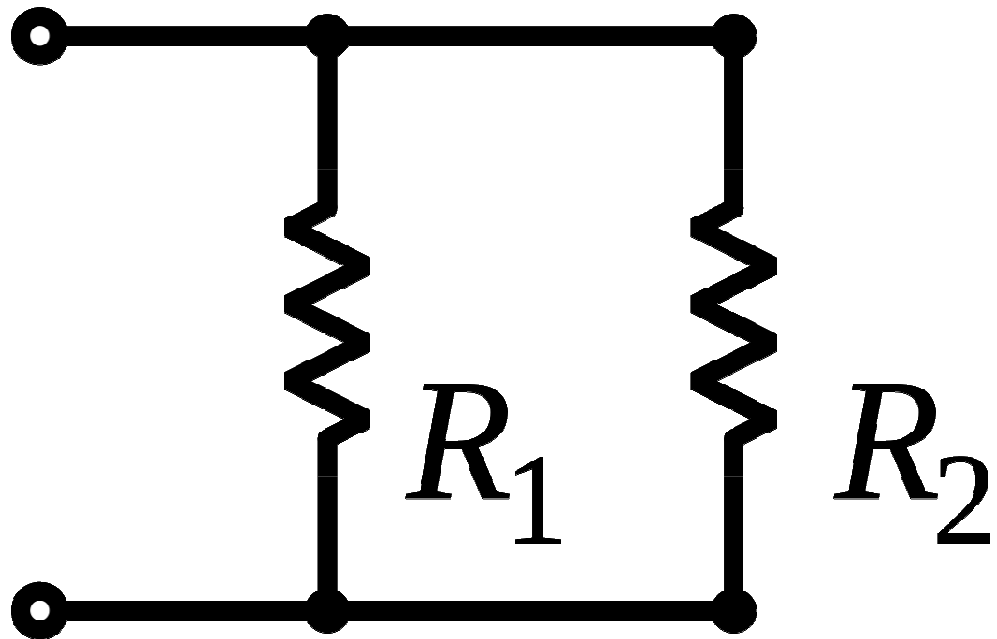

# Solution

. The equivalent resistance is given by

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

The voltage across the resistances is given by

$$v = R_{\text{eq}} i_{\text{total}} = \frac{R_1 R_2}{R_1 + R_2} i_{\text{total}}$$

Now, we can find the current in each resistance:


$$i_1 = \frac{v}{R_1} = \frac{R_2}{R_1 + R_2} i_{\text{total}}$$

# Maximum Power Transfer

- Current through load is one half of Norton equivalent current

$$P_{\max} = \frac{V_{\text{Th}}^2}{4 R_{\text{Th}}} = \frac{I_{\text{N}}^2 R_{\text{N}}}{4}$$

# Maximum Power Transfer

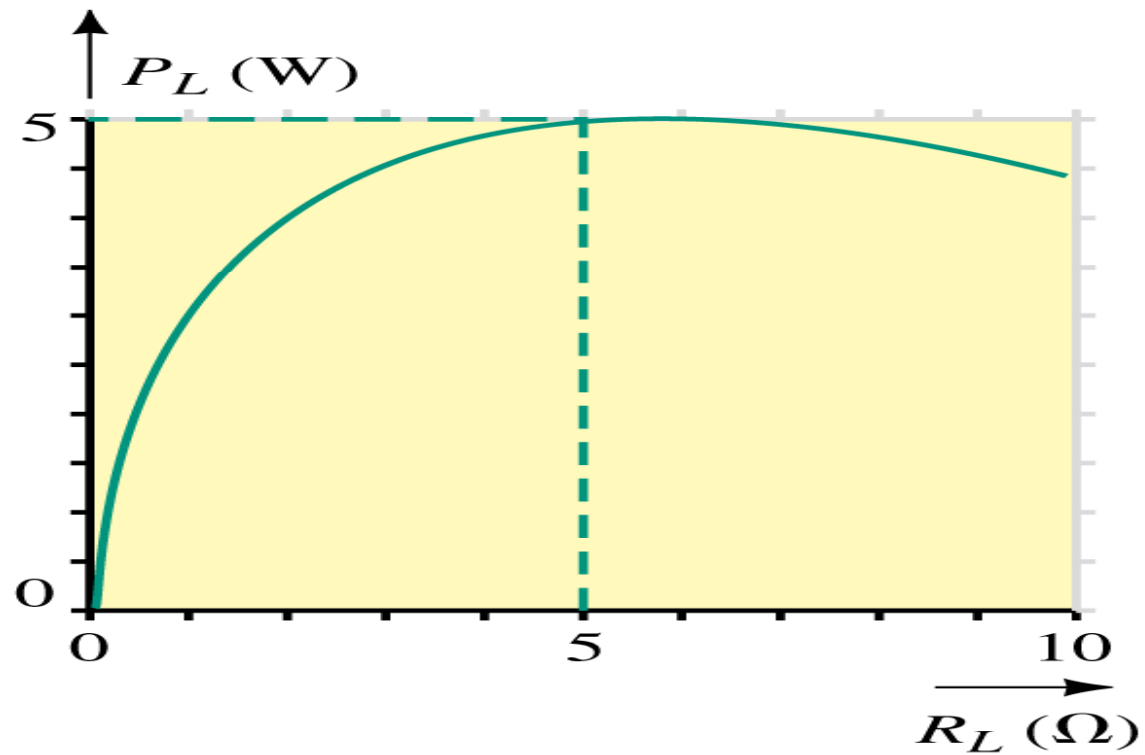

# Efficiency

- To calculate efficiency:

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

$$\eta = \frac{\frac{E_{\text{Th}}^2}{4R_{\text{Th}}}}{\frac{E_{\text{Th}}^2}{2R_{\text{Th}}}} \times 100\% = 50\%$$

# Millman's Theorem

- Used to simplify circuits that have
  - Several parallel-connected branches containing a voltage source and series resistance
  - Current source and parallel resistance
  - Combination of both

# Millman's Theorem

- Voltage sources
  - May be converted into an equivalent current source and parallel resistance using source transformation theorem
- Parallel resistances may now be converted into a single equivalent resistance

# Millman's Theorem

- **Step I:**
  - First, convert voltage sources into current sources
  - Equivalent current,  $I_{eq}$ , is just the algebraic sum of all the parallel currents



# Millman's Theorem

- **Step II:**

- Next, determine equivalent resistance,  $R_{eq}$ , the parallel resistance of all the resistors
- Voltage across entire circuit may now be calculated by:

$$E_{eq} = I_{eq} R_{eq}$$

# Millman's Theorem

- We can simplify a circuit as shown:

